

Chapter 2

Non-Linear Model

Introduction

The linear devices are those devices which follow Ohm's law ($V=IR$). In an electric circuit, a linear device is an electrical element with a linear relationship between input current & output voltage. Resistor, inductors, capacitors are example of linear devices.

The VI characteristics of linear device is a straight line.

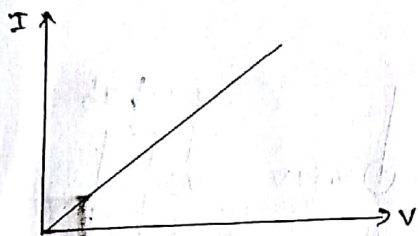


Fig: VI characteristics of a linear device

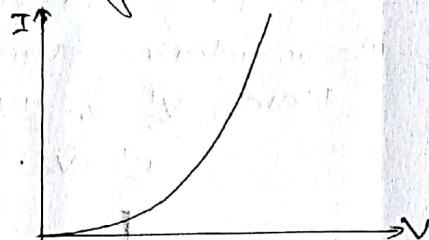


Fig: VI characteristics of non-linear devices.

The electronic devices which don't follow Ohm's law ($V \neq IR$) or whose VI characteristics is not straight line are called non-linear devices.

Properties of non-linear devices

1. They do not follow Ohm's law.
2. Their VI characteristics is not a straight line.
3. They don't follow the network theorem like Thevenin's Theorem, Norton's Theorem, superposition theorem etc.
4. The circuits containing non-linear devices can be analyzed by using KVL or KCL.
5. The internal resistance of non-linear device depends on the operating conditions like temperature, current, voltage etc.
6. Examples are: Diode, Transistors, FET etc.

Non-Linear circuit Analysis

Verify with appropriate example that non-linear device doesn't follow principle of superposition.

→ Consider a non-linear device (square-law device) whose VI characteristics eqn is given by,

$$I_S = A(V_S - V_{TR})^2 \quad \text{--- (1)}$$

where, I_S = current through non-linear device

V_S = voltage across non-linear device

V_{TR} = Threshold voltage = 0

A = constant = 1 mA/V^2

$$\text{--- then } I_S = 1 \times (V_S - 0)^2 = V_S^2 \quad \text{--- (2)}$$

Now, connect the non-linear device in a simple circuit as shown in figure.

Here, using KVL,

$$-V_1 - V_2 + V_S = 0$$

$$\Rightarrow V_S = V_1 + V_2 = 1 + 2 = 3V$$

From eqn (2),


$$I_S = V_S^2 = (3)^2 = 9mA$$

To apply superposition theorem,


1) Considering source V_1 only,

$$\text{Here, } V_S' = V_1 = 1V$$

$$I_S' = (V_S')^2 = 1mA$$

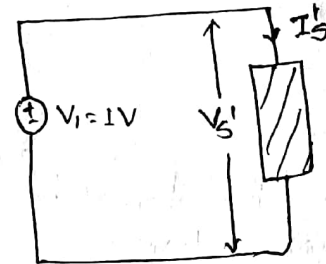

2) Considering source V_2 only,

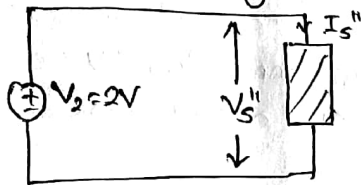

$$\text{Here, } V_S'' = V_2 = 2V$$


$$I_S'' = (V_S'')^2 = (2)^2 = 4mA$$

Now, current through a non-linear device according to superposition theorem is,

$$I_{S1} = I_S' + I_S'' = 1 + 4 = 5mA$$

Since $I_S \neq I_{S1}$, we can say that non-linear device doesn't follow principle of superposition.

For the circuit shown, find I_S & V_S .

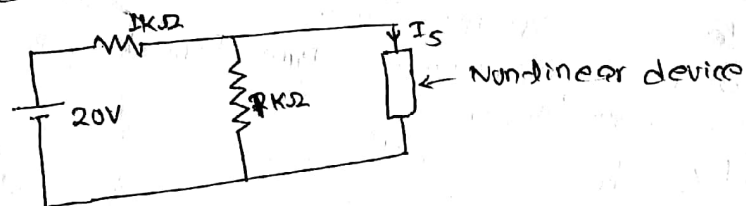


Soln: We know that,

$$I_S = A(V_S - V_{TR})^2, \text{ where,}$$

$$A = 1mA/V^2 \text{ \& } V_{TR} = 0.$$
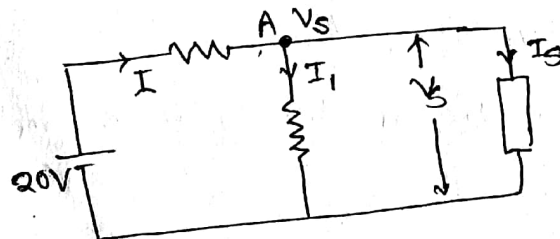
$$\therefore I_S = 1 \times (V_S - 0)^2 = V_S^2 \text{ --- (1)}$$



Applying KCL at node A,

$$I = I_1 + I_S$$

$$\text{or, } \frac{20 - V_S}{1} = \frac{V_S}{1} + I_S$$

$$\text{or, } 20 - V_S = V_S + I_S$$

$$\text{or, } 20 - V_S = V_S + V_S^2 \quad (\because \text{from eqn (1), } I_S = V_S^2)$$

$$\text{or, } V_S^2 + 2V_S - 20 = 0$$

which is quadratic in V_S .

On solving we get,

$$V_S = 3.58V \text{ or } -5.58V$$


Neglecting -ve value of V_S , we get

$$\therefore V_S = 3.58V$$

$$\text{and, } I_S = V_S^2 = (3.58)^2 = 12.82 \text{ mA}$$

Graphical Analysis of Circuit with non-linear Devices:

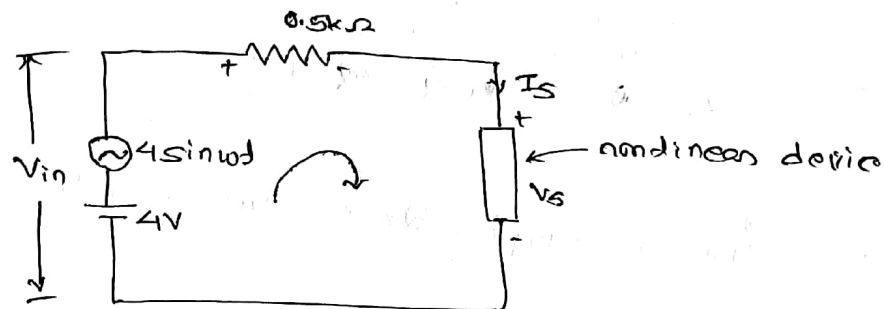* Find the operating point (or value of I_S & V_S) of non-linear device shown in circuit below. Assume $I_S = A(V_S - V_{TR})^2$ where, $A = 1 \text{ mA/V}^2$ & $V_{TR} = 0$.



$$\text{Given: } I_S = A(V_S - V_{TR})^2 = 1 * (V_S - 0)^2 = V_S^2$$

$$\Rightarrow I_S = V_S^2 \text{ — (1)}$$

To plot eqn (1) in a graph,

V_S	0	1	2	3	4
I_S	0	1	4	9	16

Applying KVL in given circuit,

$$4 + 4 \sin \omega t - 0.5 I_S - V_S = 0$$

$$\text{or, } 4 + 4 \sin \omega t = 0.5 I_S + V_S$$

$$\Rightarrow 8 + 8 \sin \omega t = I_S + 2V_S \text{ — (2)}$$

Take $\omega t = \pi/2$,

$$\text{Then, } 8 + 8 \sin \pi/2 = I_S + 2V_S$$

$$\text{or, } 8 + 8 = I_S + 2V_S$$

$$\Rightarrow 16 - 2V_S = I_S \text{ — (3)}$$

To plot eqn (3) on graph,

I_S	14	12	10	8	6	16	0
V_S	1	2	3	4	5	0	8

Again, take $\omega t = \pi$


Then, $8 + 8 \sin \pi = I_S + 2V_S$

or, $8 = I_S + 2V_S$

or, $I_S = 8 - 2V_S$ — (4)

To plot eqn (4) on graph,

I_S	8	6	4	2	0
V_S	0	1	2	3	4

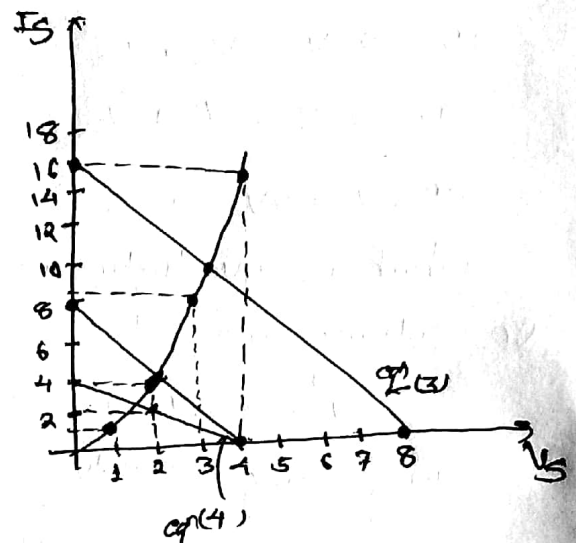

Take $\omega t = 3\pi/2$

Then, $8 + 8 \sin(3\pi/2) = I_S + 2V_S$

or, $8 + 8(-1) = I_S + 2V_S$

$\Rightarrow I_S = -2V_S$ — (5)

To plot eqn (5) in graph,

I_S	0	-2	2	-4	4	-6	6
V_S	0	1	-1	2	-2	3	-3

Now, from a graph, Q_2 is the operating point.

Thus, $V_S = 2V$
& $I_S = 2mA$.

Diode as a Non-linear Device

The device which does not follow Ohm's law ($V=IR$) or whose $V-I$ characteristic curve is not a straight line is called a non-linear device.

For a diode, the voltage-current relation is given by

$$I = I_S (e^{\frac{V}{\eta V_T}} - 1)$$

where, I_S = reverse (leakage) saturation current

η = constant ($1 \leq \eta \leq 2$)

V_T = thermal voltage

Diode is a nonlinear device because diode does not have a linear relationship betⁿ current & voltage. Diode are called non-linear devices because they possess the properties of non-linear devices. (which are described earlier).


Piecewise Linear Model of a Diode

Ideal Model

Forward biased diode \rightarrow short circuit (closed switch)

Reverse biased diode \rightarrow open circuit (open switch)

Barrier potential = 0

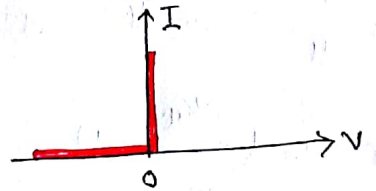

Piecewise Linear Model

The V - I relationship for a diode is given by

$$I = I_s (e^{\eta V / m V_T} - 1) \quad (1)$$

Where, I_s = reverse saturation current

η = constant ($1 \leq \eta \leq 2$)

If we plot above eqn, we get a non-linear characteristics as shown in figure below

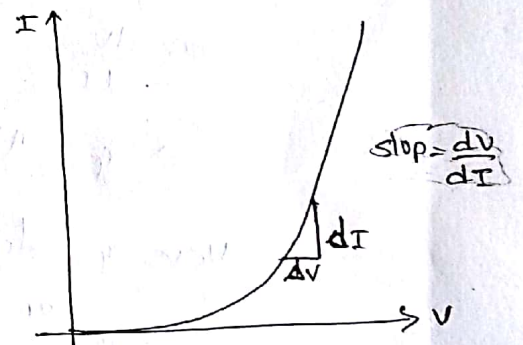


Fig: V - I characteristics of a diode.

In piecewise linear modeling of the diode, we represent the above non-linear characteristics by two straight lines OA & AB as shown in figure below.

Equation of line OA:

$$I = 0 \text{ for } V < V_f$$

Equation of line AB:

$$I = \frac{V - V_f}{r_f} \text{ for } V > V_f$$


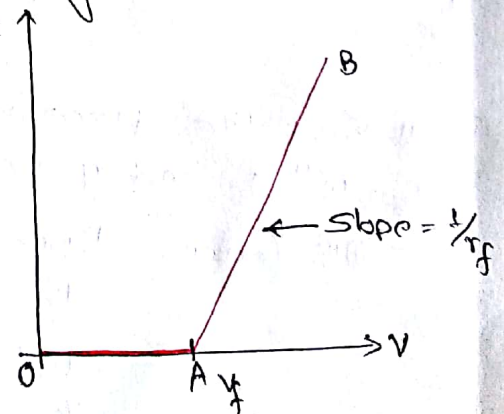


Fig: piecewise linear model of a diode.

Thus we represent the non-linear characteristics of diode in piecewise linear model as,

$$I = \begin{cases} 0 & \text{for } V < V_f \\ \frac{V - V_f}{r_f} & \text{for } V > V_f \end{cases}$$

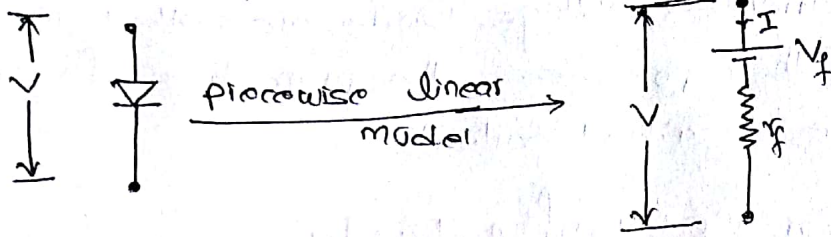So, we can represent a diode in piecewise linear model as,



We know that,

$$\text{slope} = \frac{1}{r_f}$$

$$\text{or, } \frac{dI}{dV} = \frac{1}{r_f} \Rightarrow r_f = \frac{dV}{dI} \quad (1)$$

We have, $I = I_s (e^{\frac{V}{\eta V_T}} - 1)$

$$\text{or, } I = I_s e^{\frac{V}{\eta V_T}} \quad (\because \text{neglecting } 1)$$

On differentiating wrt to V

$$\frac{dI}{dV} = I_s \cdot \frac{1}{\eta V_T} \cdot e^{\frac{V}{\eta V_T}} = \frac{I_s e^{\frac{V}{\eta V_T}}}{\eta V_T} = \frac{I}{\eta V_T}$$

$$\text{or, } \frac{dV}{dI} = \frac{\eta V_T}{I}$$

$$\Rightarrow r_f = \frac{\eta V_T}{I}$$

Here, r_f = forward diode resistance or air resistance or dynamic resistance.

Also, from above fig,

$$V = I \cdot r_f + V_f$$

$$\therefore V_f = V - I \cdot r_f$$

Find the piecewise linear model of a diode (silicon) with $I_s = 10^{-11} \text{ A}$ and $\eta = 1.6$ in the vicinity of operating point, $I = 1 \text{ mA}$.

Soln: Given, Diode current (I) = $1 \text{ mA} = 1 \times 10^{-3} \text{ A}$


$$I_s = 10^{-11} \text{ A}$$

$$\eta = 1.6$$

$$r_f = ?$$

$$V_f = ?$$

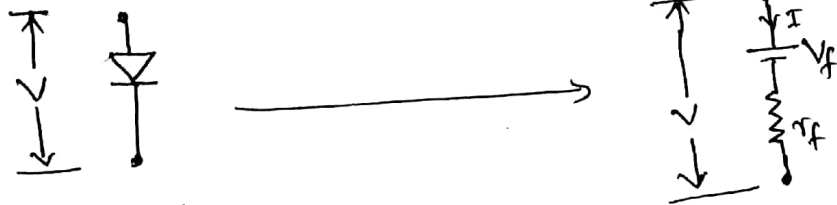The piecewise linear model of a diode is,



We know that,

$$\text{forward diode resistance, } r_f = \frac{\eta V_T}{I} = \frac{1.6 \times 0.026}{1 \times 10^{-3}} = 41.6 \Omega$$

$$\text{Also, } V_f = V - I * r_f \quad \text{--- (1)}$$

We know that,

$$I = I_S (e^{V/\eta V_T} - 1)$$

$$\text{or, } \frac{I}{I_S} = e^{V/\eta V_T} - 1$$

$$\text{or, } \frac{1 \times 10^{-3}}{10^{-11}} = e^{V/(1.6 \times 0.026)} - 1$$

$$\text{or, } 10^8 + 1 = e^{V/0.0416}$$

$$\text{or, } \ln(10^8 + 1) = \frac{V}{0.0416}$$

$$\text{or, } V = 0.0416 * 18.42$$

$$\therefore V = 0.766 \text{ V}$$

Again from eqⁿ (1),

$$V_f = V - I * r_f = 0.766 - 10^{-3} * 41.6 = 0.766 - 0.0416$$

$$\therefore V_f = 0.723 \text{ V}$$